Objective:


To design a regular circuit

Theony:

A negister is a group of binny cells suitable Jon including binary information. The information stoud william the registors can be transferred with the help e) shift registers. Shift registers are a group of slip-slopes used to stone multiple bits of data. The bits stond in such ryshes can be made to move within and infort of registers through clock pulses

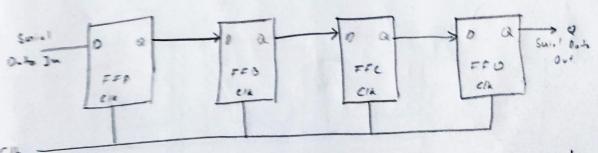
## Social In Swid Out Register (5150)

The circuit consists of your D- Slip glaps connected in a serial manner. All the flip flops are synchronious with each other since the same clock signal is provided to each flip flop. The main use of 5150 registor is as a delay element



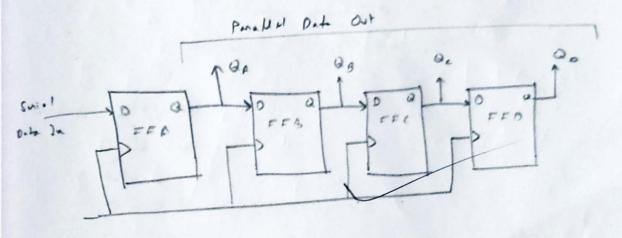
## Sorial In Parallel Out Register (5100)

This shift register allows social input ( one bit after the other through a single data hime) and produces a parablel output is known as social In Parablel out register. The main use of SIPO register: to convert Social Data into Parablel Outa.



Prakled In Paraklet Out Register (PIPO)

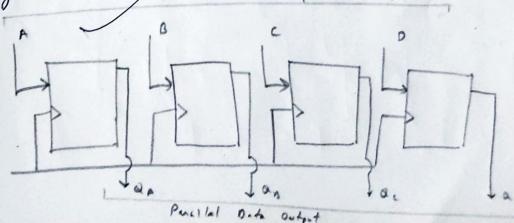The shift register which allows parable import to each slip slop (separately) and in a simultaneous manner and also produces a penable out put is called Panable In also produces a penable out put is called Panable In Ponable Out shift register. Its main use is as a temporary storage device penable Data Japat



Pin Dingram:

Matrids Required:

- · Digital Trainer Kit
- · Wins
- · Dud D Flip-Flop (164013) x2

Verification Table:

Serial In Swind Out Register

CIL	CIK	Swial Data Injut (D)	Social Data Output (a)
	0	1	0
	1	0	0
	2	0	o
	3	0	0
	4	0	1
	5	0	O

-	Swid pata Injut (1)	Pana	Mil	Data (	Duffe
9	0	Q,	a,	Q.	a.
1	0	0	0	D	0
2		1	0	. 0	0
3		0	1		0
4		0	0	1	0
5	0	0	0	0	1
		0	0	0	0

#### Prohable In Parallel Out Registon

clk	Paralla	d Da	ta Iv	pot	Para	Parallel Data Output				
	A	1 3	10	0	Q.	QB	0.	0.		
0	0	0	0	0	0	٥	0	9		
1	1	0	0	0	1	0	s	0		
2	0	0	0			1				
3	0	0	0	٥	0	0	0	0		
4	0	0 .	٥	0	0	0	6	1		
5	0	0	0	0	0		0	0		

### Conclusion:

Registors are a very widely used component and a very integral part of modern day electronics with its applications in nanging from holding data instructions and memory address in a cou to lighting components as well as telecommunication dvices.

# ADDER - SUBTRACTOR


objective:


To design an addir-subhactor composite circuit.
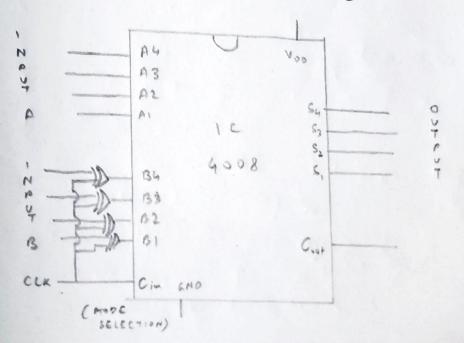
#### Theory:

An odder - subtraction cinevit is a Ligital cinevit that performs both addition and subtraction of binary numbers. The Adelin - Subtractor cincuit is also known as the orithmetic and togic unit and is an exential component of a computer.

It is a variable component capable of performing noth addition and subtraction in a very cost effective solution on a vay easy to design circuits whose wer uses are widespread in digital systems.



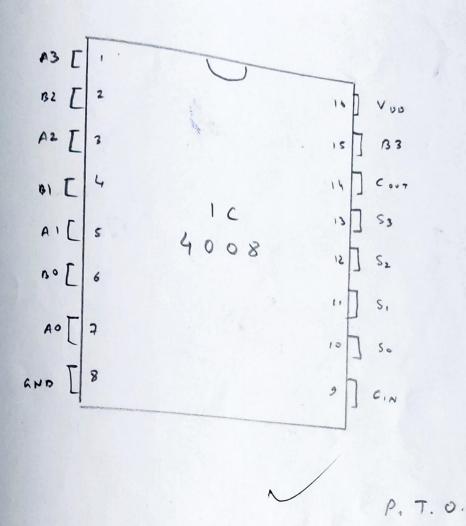

14

Megrind:

I [hu	Specification	aty.
Digital Trainer	Kit In constructing ci	nevit 1
	for horspring the	h 1
Wins	signam	1
10 4070 ( xon)	4 × 2-6it ×or op	
1 c 4008 ( Addu - Subtractor con	completed IC with	1
( Adu- Subtractor cos	posite) meassay operations for addition-subtree	k.~

Julia Table:

	INPUT							OUTPUT					
de	As	Az			134	B3	B,	В,	Su	53	52	S,	(0
	0	0	1	-	0	0	1	0	0	ı	0	(	0
dd	0	0	ι	. (	0	0	1	0	0	0	0	1	1
du;				,	0	0	0	1	1	ι	0	0	0
Add	1	0	1		0				0	0	0	1	1
504	0	1	١	0	0	(		'					
						1							

inclusion:

Adden- Eustracton circuit is an enoutial component of digital systems and used in many applications such as dyted computers, digital signal procursing systems etc. His a valuable component you any digital system and in the field of digital electronics.